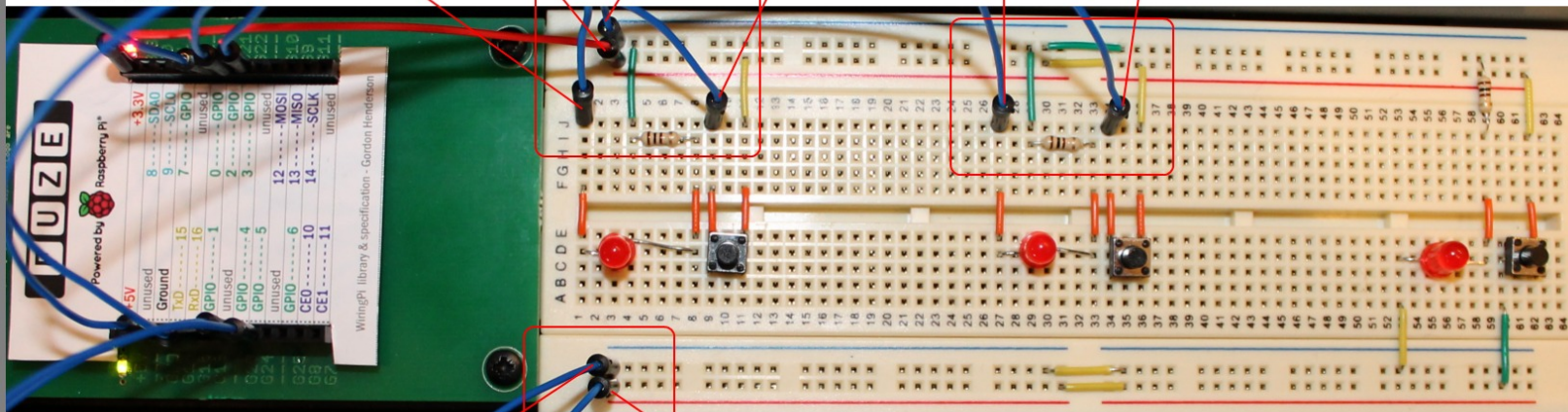


# FUZE®

Get with  
the PROGRAM

[www.fuze.co.uk](http://www.fuze.co.uk)



GPIO 0

+3.3V

GROUND

GPIO 1

GPIO 2

GPIO 3

From the FUZE  
Component Kit

3 x 100R Resistors

3 x LED

3 x microswitch button

GPIO 4

GPIO 5

# REACTION RACER